

銘傳大學九十二學年度資訊傳播工程約系碩士班招生考試

第二節

電子學 試題

- (a) (5%) Please plot the circuit symbols of a diode, a bipolar p-n-p type transistor and an n-channel MOS FET.

(b) (15%) In Fig. P1, find the output voltage ($V_{BE(active)=0.7 V}$) for input (V_i) levels of 0.2V and 12V, respectively. The silicon $h_{FE}=50$, transistor in the figure has characteristics as follows:

$$V_{CE(sat)}=0.2 V, V_{BE(sat)}=0.8 V, V_{BE(active)}=0.7 V, V_{BE(active)}=0.5 V, V_{BE(cutoff)}=0.0 V$$
- (a) (5%) Please plot the circuit symbols and list truth tables of NAND, NOR, and XOR gate, respectively.

(b) (15%) Find the simplest two level NAND circuit which will realize the function $f(A, B, C, D) = ABC' + AD' + BC'D + AB'D + ACD$.
- (a) (5%) Please plot the logic symbols and list the characteristic tables of the JK, T, and D flip-flops, respectively.

(b) (15%) Design a sequential circuit whose state diagram is shown in Fig. P3. Use T flip-flops and logic gates.
- (a) (5%) Please list characteristics of an ideal OP amplifier.

(b) (15%) Please derive an expression for output voltage V_o of the circuit shown in Fig. P4. Assume the OP AMP in the figure is ideal.
- (a) (10%) Explain the early effect (base-width modulation). Explain qualitatively the three consequences of this effect.

(b) Describe the Hall effect. What properties of a semiconductor are determined from a Hall effect experiment?

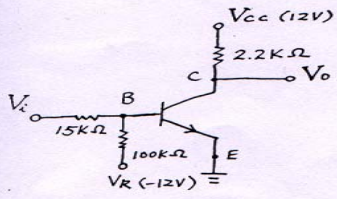


Fig. P1

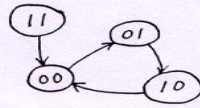


Fig. P3

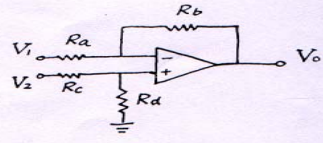


Fig. P4

试题完