

電子學 試題 (限用答案本作答)

可使用計算機

一、單選選擇題 (每題四分, 共六十分)

1. ( ) In a common-source amplifier, the output voltage is (a)  $180^\circ$  out of phase with the input (b) in phase with the input (c) taken at the source (d) taken at the drain (e) answers (a) & (c) (f) answers (a) and (d)
2. ( ) A common source amplifier has a load resistance of  $10k\Omega$  and  $R_D=820\Omega$ . If  $g_m=5\text{ mS}$  and  $V_{in}=500\text{mV}$ , the output signal voltage is (a)  $1.89\text{ V}$  (b)  $2.05\text{V}$  (c)  $25\text{V}$  (d)  $0.5\text{V}$
3. ( ) The common-gate amplifier differs from both the common-source and common-drain configurations in that it has a (a)much higher voltage gain (b)much lower voltage gain (c)much higher input resistance (d) much lower input resistance
4. ( ) Determine the Miller INPUT capacitance in Figure 1. (a)  $812\text{pF}$  (b)  $912\text{pF}$  (c)  $4\text{pF}$  (d)  $10\text{ pF}$
5. ( ) Determine the Miller OUTPUT capacitance in Figure 1. (a)  $812\text{pF}$  (b)  $912\text{pF}$  (c)  $4\text{pF}$  (d)  $10\text{ pF}$
6. ( ) In a step response test of a certain amplifier, rise time  $t_r=20\text{ns}$ . What is critical upper frequency  $f_{cu}$  (a)  $116\text{MHz}$  (b)  $13.5\text{MHz}$  (c)  $17.5\text{MHz}$  (d)  $146\text{MHz}$
7. ( ) A certain transistor has an unity frequency ( $f_T$ ) of  $175\text{MHz}$ . When this transistor is used in an amplifier with a midrange voltage gain of 50, what bandwidth can be achieved ideally (a)  $175\text{MHz}$  (b)  $3.5\text{MHz}$  (c)  $17.5\text{MHz}$  (d)  $146\text{MHz}$
8. ( ) Determine the  $V_{out}(\text{max})=?\text{V}$  of Figure 2 (a)  $11.4$  (b)  $-11.4$  (c)  $-7.94$  (d)  $7.94$  (e) none in above

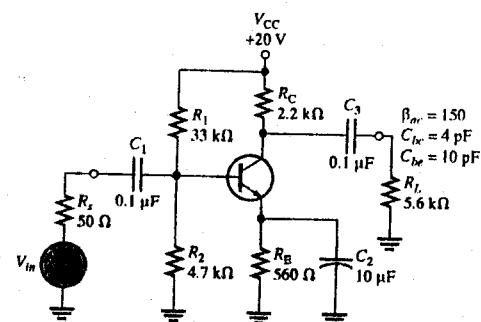


Figure 1

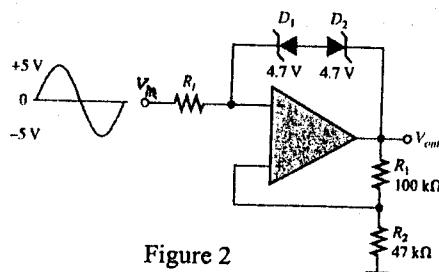


Figure 2

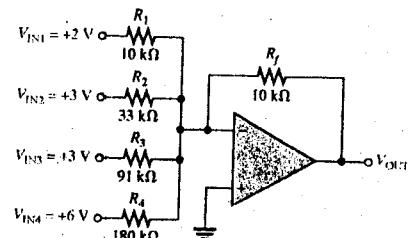


Figure 3

9. ( ) In figure 3, find the output voltage when the input voltage are applied to the scaling adder.? V (a)  $3.57$  (b)  $-3.57$  (c)  $3.23$  (d)  $-3.23$  (e) none in above
10. ( ) In figure 3, what is the current ( $\mu\text{A}$ ) through  $R_f$  (a)  $35.7$  (b)  $357$  (c)  $3.57$  (d)  $75.3$  (e) none in above
11. ( ) determine the center frequency of figure  $47\text{ kHz}$  (a)  $3.39$  (b)  $7.23$  (c)  $45$  (d)  $4.95$

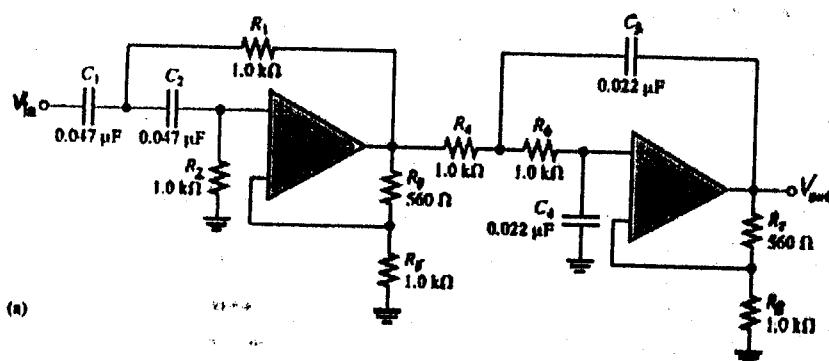


figure 4

電子學 試題 (限用答案本作答)

- 12.( ) Discuss the low-frequency response of the BJT amplifier in figure 5. The critical frequency of input network of  $C_1$  is  
 (a) 578Hz (b) 6.89kHz (c) 177Hz (d)  
 410Hz (e) 102kHz

- 13.( ) In figure 5, the critical frequency of output network of  $C_3$  is (a) 578Hz (b)  
 6.89kHz (c) 177Hz (d) 410Hz (e) 102kHz

- 14.( ) In figure 5, the critical frequency of bypass network of  $C_2$  is (a) 578Hz (b)  
 6.89kHz (c) 177Hz (d) 410Hz (e) 102kHz

- 15.( ) What is the voltage gain of figure 5 (a)34.7 (b)86.6 (c)66.7 (d)90.1

二、非選擇題(共四十分)

1. Drawing the  $R_L$  waveform for each circuit and indicate the peak values. (Assume voltage drop is 0.7 when diode forward bias). (10 分)

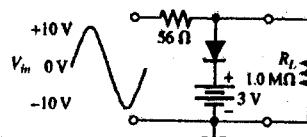


Figure 6 (a)

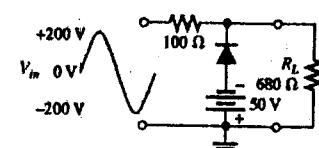


figure 6(b)

2. Determine transistor terminal voltages  $V_B$  in figure 7 with respect to ground and  $I_C$ . Do not neglect the input resistance at the base or  $V_{BE}$  (10 分)

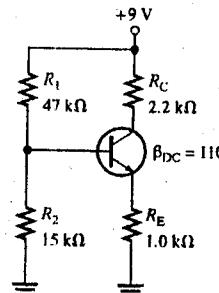


Figure 7

3. In Figure 8, find  $R_{in}=? \Omega$  and find  $A_v(V_{out}/V_{in})=?$  Current gain=? Power gain=? (20 分)

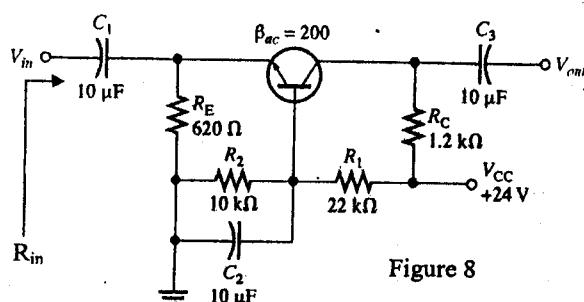


Figure 8

本試題兩面印刷

試題完